

# Lab 01-gates

---

## Verification of De Morgan's laws

---

### Results table

c	b	a	f(c,b,a)
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

[Link to EDA Playground project](#)

### Source VHDL code from *design.vhd*

```
library ieee;                -- Standard library
use ieee.std_logic_1164.all; -- Package for data types and logic operations

-----
-- Entity declaration for basic gates
-----

entity gates is
  port(
    a_i      : in  std_logic;    -- Data input
    b_i      : in  std_logic;    -- Data input
    c_i      : in  std_logic;    -- Data input
    f_o      : out std_logic;    -- base output function
    f_nand_o : out std_logic;    -- NAND output function
    f_nor_o  : out std_logic;    -- NOR output function
```

```

    );
end entity gates;


-----
-- Architecture body for basic gates
-----

architecture dataflow of gates is
begin
    f_o      <= (not b_i and a_i) or (not c_i and not b_i);
    f_nand_o  <= not (not (not b_i and a_i) and not(not b_i and not c_i));
    f_nor_o   <= not (b_i or not a_i) or not (c_i or b_i);

end architecture dataflow;

```

## Simulation screenshot

 

## Verification of Distributive laws

[Link to EDA Playground project](#)

## Source VHDL code from *design.vhd*

```

library ieee;                -- Standard library
use ieee.std_logic_1164.all; -- Package for data types and logic operations

-----
-- Entity declaration for basic gates
-----

entity gates is
    port(
        a_i      : in  std_logic;    -- Data input
        b_i      : in  std_logic;    -- Data input
        c_i      : in  std_logic;    -- Data input
        f_or_left_o : out std_logic;  -- OR LEFT SIDE output functi
        f_or_right_o : out std_logic; -- OR LEFT SIDE output functi
        f_and_left_o : out std_logic;  -- AND LEFT SIDE output funct

```

```

        f_and_right_o          : out std_logic          -- AND RIGHT SIDE output func
    );
end entity gates;

-----
-- Architecture body for basic gates
-----

architecture dataflow of gates is
begin
    f_or_left_o      <= (a_i and b_i) or (a_i and c_i);
    f_or_right_o     <= a_i and (b_i or c_i);
    f_and_left_o     <= (a_i or b_i) and (a_i or c_i);
    f_and_right_o    <= a_i or (b_i and c_i);

end architecture dataflow;

```

## Simulation screenshot

