

# Lab 04-segment

## 1. Preparation tasks

Decoder truth table for common anode 7-segment display

Hex	Inputs	A	B	C	D	E	F	G
0	0000	0	0	0	0	0	0	1
1	0001	1	0	0	1	1	1	1
2	0010	0	0	1	0	0	1	0
3	0011	0	0	0	0	1	1	0
4	0100	1	0	0	1	1	0	0
5	0101	0	1	0	0	1	0	0
6	0110	0	1	0	0	0	0	0
7	0111	0	0	0	1	1	1	1
8	1000	0	0	0	0	0	0	0
9	1001	0	0	0	0	1	0	0
A	1010	0	0	0	1	0	0	0
b	1011	1	1	0	0	0	0	0
C	1100	0	1	1	0	0	0	1
d	1101	1	0	0	0	0	1	0
E	1110	0	1	1	0	0	0	0
F	1111	0	1	1	1	0	0	0

Table with connection of 7-segment displays on Nexys A7 board

SW	AN	SW PIN	AN PIN	7-seg LED	7-seg PIN
SW0	AN7	J15	U13	CA	T10

SW	AN	SW PIN	AN PIN	7-seg LED	7-seg PIN
SW1	AN6	L16	K2	CB	R10
SW2	AN5	M13	T14	CC	K16
SW3	AN4	R15	P14	CD	K13
SW4	AN3	R17	J14	CE	P15
SW5	AN2	T18	T9	CF	T11
SW6	AN1	U18	J18	CG	L18
SW7	AN0	R13	J17	DP	H15

## 2. Seven-segment display decoder

---

VHDL architecture from source file hex\_7seg.vhd

```

architecture Behavioral of hex_7seg is
begin
    p_7seg_decoder : process(hex_i)
    begin
        case hex_i is
            when "0000" =>
                seg_o <= "0000001"; -- 0
            when "0001" =>
                seg_o <= "1001111"; -- 1
            when "0010" =>
                seg_o <= "0010010"; -- 2
            when "0011" =>
                seg_o <= "0000110"; -- 3
            when "0100" =>
                seg_o <= "1001100"; -- 4
            when "0101" =>
                seg_o <= "0100100"; -- 5
            when "0110" =>
                seg_o <= "0100000"; -- 6
            when "0111" =>
                seg_o <= "0001111"; -- 7
            when "1000" =>
                seg_o <= "0000000"; -- 8
            when "1001" =>
                seg_o <= "0000100"; -- 9
            when "1010" =>
                seg_o <= "0001000"; -- A
            when "1011" =>
                seg_o <= "1100000"; -- b
            when "1100" =>
                seg_o <= "0110001"; -- C
        end case;
    end process;
end Behavioral;

```

```

when "1101" =>
    seg_o <= "1000010"; -- d
when "1110" =>
    seg_o <= "0110000"; -- E
when others =>
    seg_o <= "0111000"; -- F
end case;
end process p_7seg_decoder;

```


## VHDL stimulus process from testbench file tb\_hex\_7seg.vhd

```

p_7seg_decoder : process
begin
    report "Stimulus process started" severity note;
    s_hex <= "0000"; wait for 100 ns;
    s_hex <= "0001"; wait for 100 ns;
    s_hex <= "0010"; wait for 100 ns;
    s_hex <= "0011"; wait for 100 ns;
    s_hex <= "0100"; wait for 100 ns;
    s_hex <= "0101"; wait for 100 ns;
    s_hex <= "0110"; wait for 100 ns;
    s_hex <= "0111"; wait for 100 ns;
    s_hex <= "1000"; wait for 100 ns;
    s_hex <= "1001"; wait for 100 ns;
    s_hex <= "1010"; wait for 100 ns;
    s_hex <= "1011"; wait for 100 ns;
    s_hex <= "1100"; wait for 100 ns;
    s_hex <= "1101"; wait for 100 ns;
    s_hex <= "1110"; wait for 100 ns;
    s_hex <= "1111";
    report "Stimulus process finished" severity note;
    wait;
end process p_7seg_decoder;

```
 
## Screenshot with simulated time waveforms



## VHDL code with 7-segment module instantiation from source file top.vhd

```

hex2seg : entity work.hex_7seg
port map(
    hex_i    => SW,

```

```

        seg_o(6) => CA,    -- 6 MSB
        seg_o(5) => CB,
        seg_o(4) => CC,
        seg_o(3) => CD,
        seg_o(2) => CE,
        seg_o(1) => CF,
        seg_o(0) => CG
    );

```

### 3. LED(7:4) indicators

---

Truth table for LEDs(7:4)

Hex	Inputs	LED4	LED5	LED6	LED7
0	0000	1	0	0	0
1	0001	0	0	1	1
2	0010	0	0	0	1
3	0011	0	0	1	0
4	0100	0	0	0	1
5	0101	0	0	1	0
6	0110	0	0	0	0
7	0111	0	0	1	0
8	1000	0	0	0	1
9	1001	0	0	1	0
A	1010	0	1	0	0
b	1011	0	1	1	0
C	1100	0	1	0	0
d	1101	0	1	1	0
E	1110	0	1	0	0
F	1111	0	1	1	0

### VHDL code for LEDs(7:4)

```
LED(3 downto 0) <= SW;
```

```

LED (4) <= '1' when (SW = "0000") else '0'; -- 0

LED (5) <= '1' when (SW > "1001") else '0'; -- > 9

LED (6) <= '1' when (SW(0) = '1') else '0'; -- 1, 3, 5, 7, 9...

LED (7) <= '1' when (SW = "0001") else -- 1, 2, 4, 8...
         '1' when (SW = "0010") else
         '1' when (SW = "0100") else
         '1' when (SW = "1000") else '0';

```

Screenshot with simulated time waveforms

